

# A/D and D/A lab experiment


# 1 experiment (+1 optional)

---


- Implement a scale
  - PSoC
  - Load cell (based on a strain guage)
  - Instrumentation amplifier
- Optional: Experiment with the PSoC WaveDAC

# Load cell

---

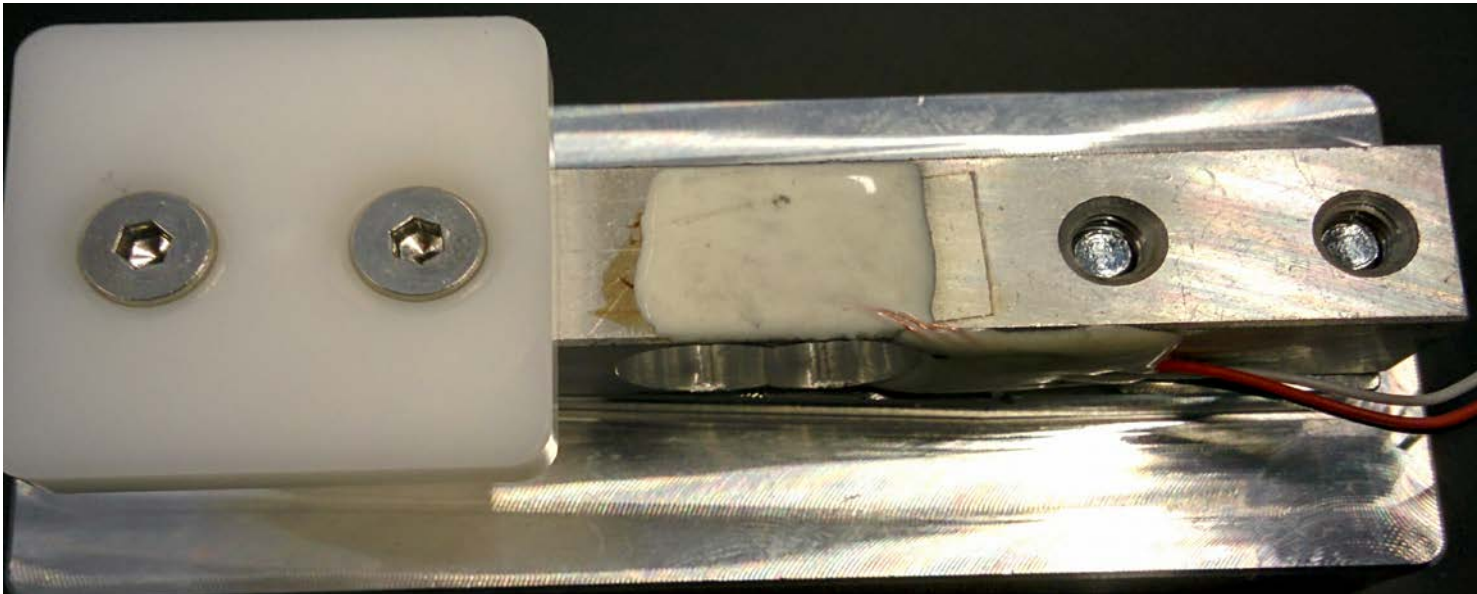


# Strain gauge

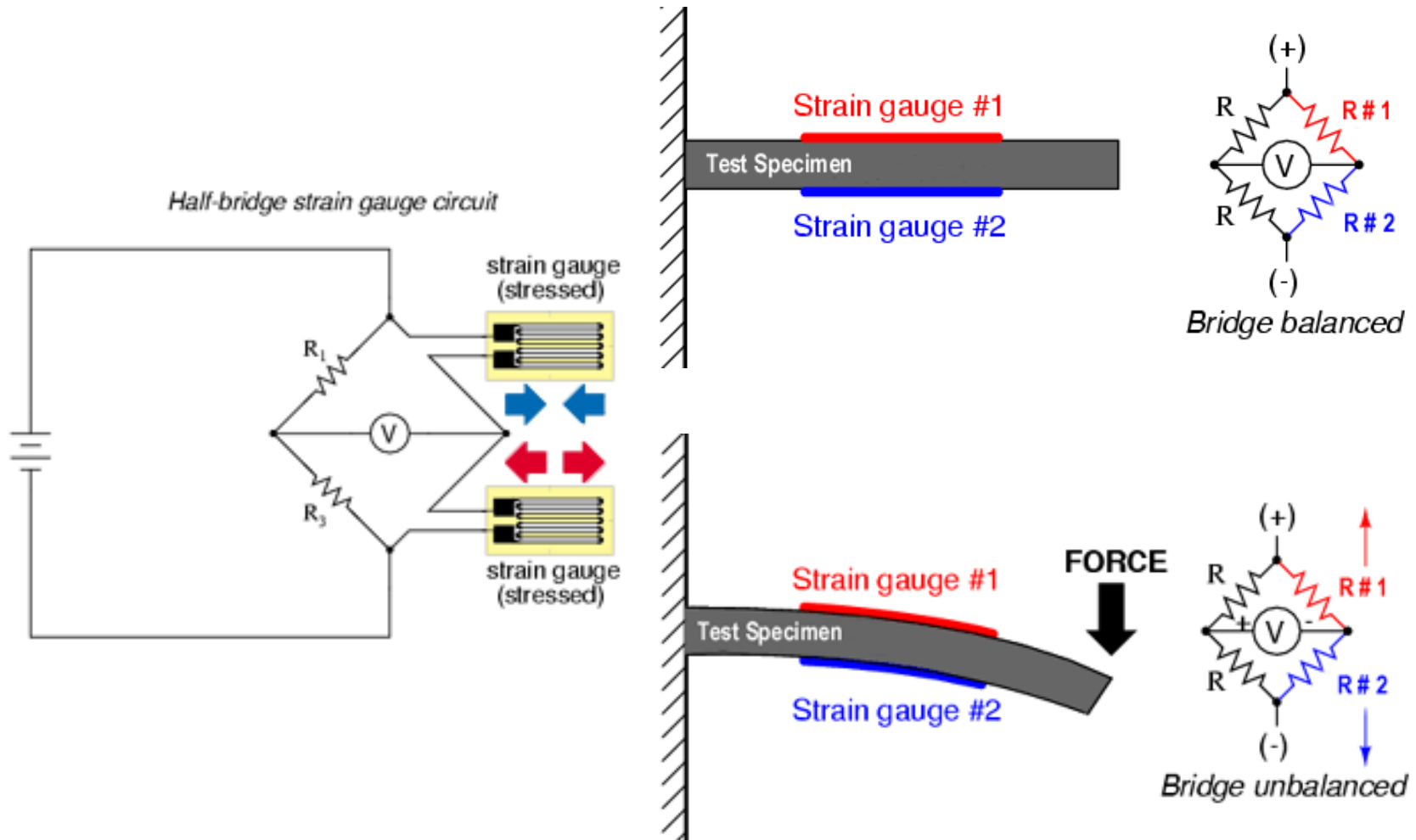


# Strain gauge based weight in lab

---

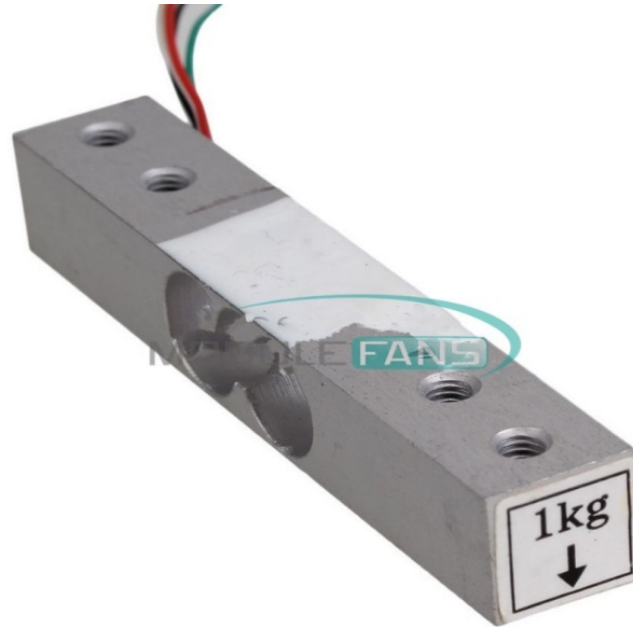

- Datasheet on blackboard.
- Based on a half bridge strain gauge.
- Range: 0-1 kg
- Output signal approximately 1mV/V.

# AD620 Instrumentation AMP

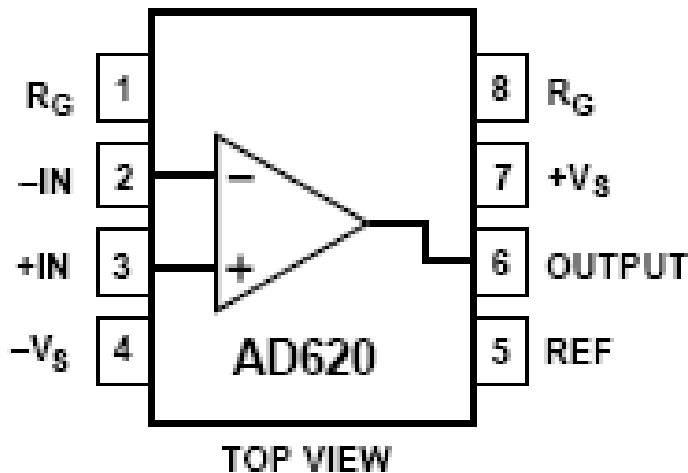

## FEATURES

### EASY TO USE

Gain Set with One External Resistor

(Gain Range 1 to 1000)

Wide Power Supply Range ( $\pm 2.3$  V to  $\pm 18$  V)

Higher Performance than Three Op Amp IA Designs

Available in 8-Lead DIP and SOIC Packaging

Low Power, 1.3 mA max Supply Current

### EXCELLENT DC PERFORMANCE ("B GRADE")

50  $\mu$ V max, Input Offset Voltage

0.6  $\mu$ V/ $^{\circ}$ C max, Input Offset Drift

1.0 nA max, Input Bias Current

100 dB min Common-Mode Rejection Ratio ( $G = 10$ )

### LOW NOISE

9 nV/ $\sqrt{\text{Hz}}$ , @ 1 kHz, Input Voltage Noise

0.28  $\mu$ V p-p Noise (0.1 Hz to 10 Hz)

### EXCELLENT AC SPECIFICATIONS

120 kHz Bandwidth ( $G = 100$ )

15  $\mu$ s Settling Time to 0.01%

### APPLICATIONS

Weigh Scales


ECG and Medical Instrumentation

Transducer Interface

Data Acquisition Systems


Industrial Process Controls

Battery Powered and Portable Equipment

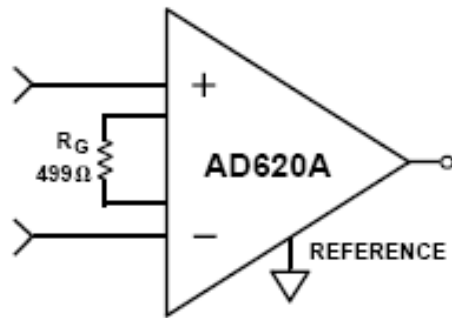

AD620A MONOLITHIC  
INSTRUMENTATION  
AMPLIFIER,  $G = 100$

SUPPLY CURRENT = 1.3mA MAX

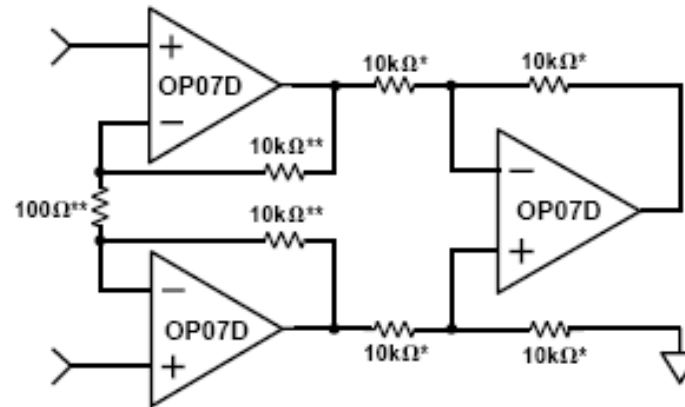

"HOMEBREW" IN-AMP,  $G = 100$


\*0.02% RESISTOR MATCH, 3PPM/°C TRACKING

\*\*DISCRETE 1% RESISTOR, 100PPM/°C TRACKING

SUPPLY CURRENT = 15mA MAX

- The AD620 is a complete instrumentation amplifier in a single package.

# Setting the gain

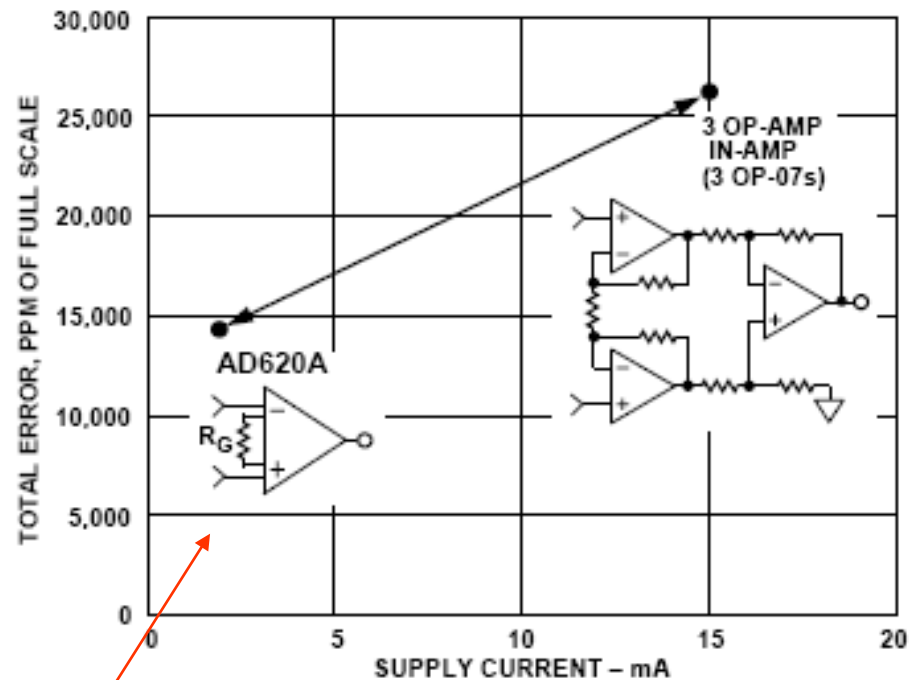


$$G = \frac{49.4 \text{ k}\Omega}{R_G} + 1$$

so that


$$R_G = \frac{49.4 \text{ k}\Omega}{G - 1}$$




# Load cell AMP PCB

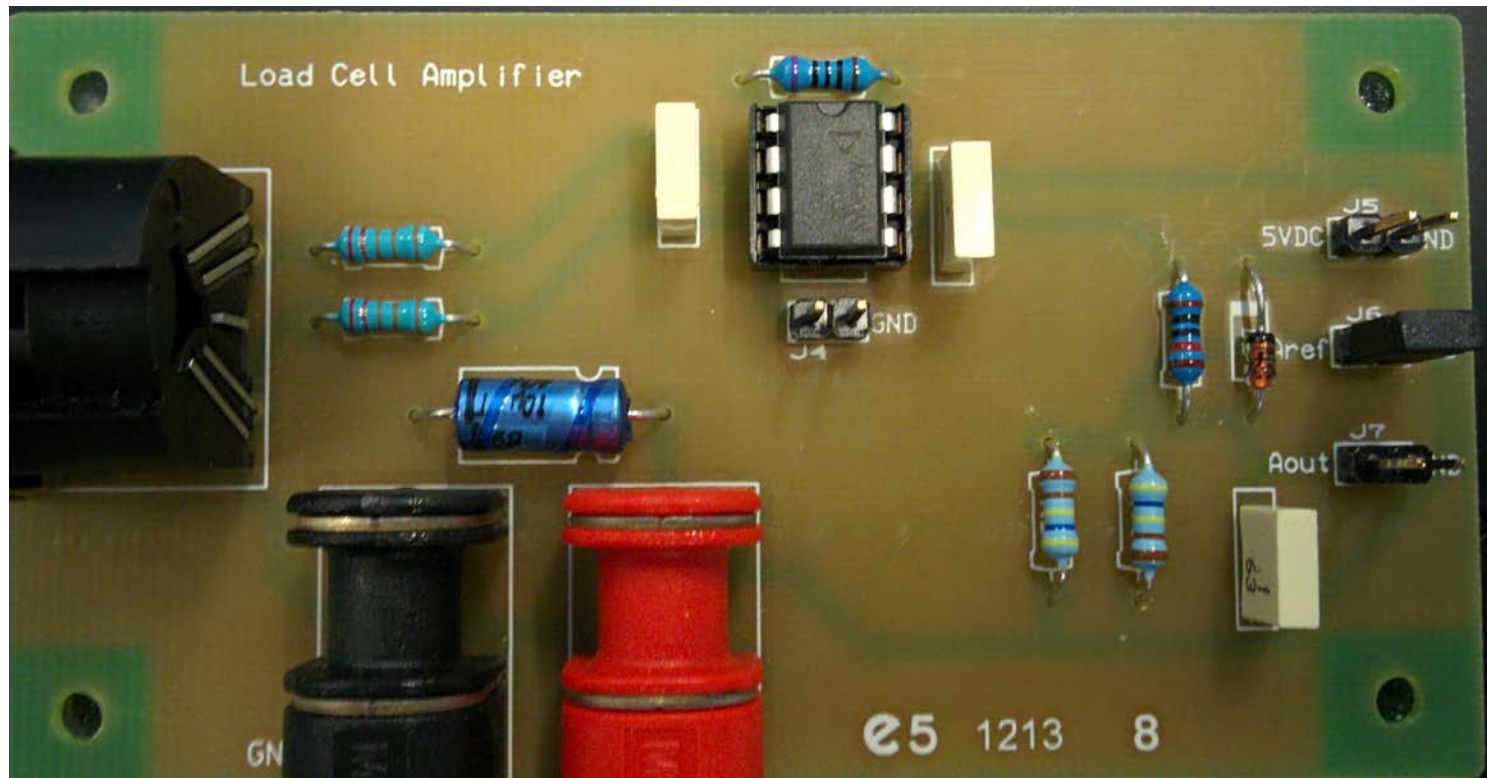


# Load cell interface PCB

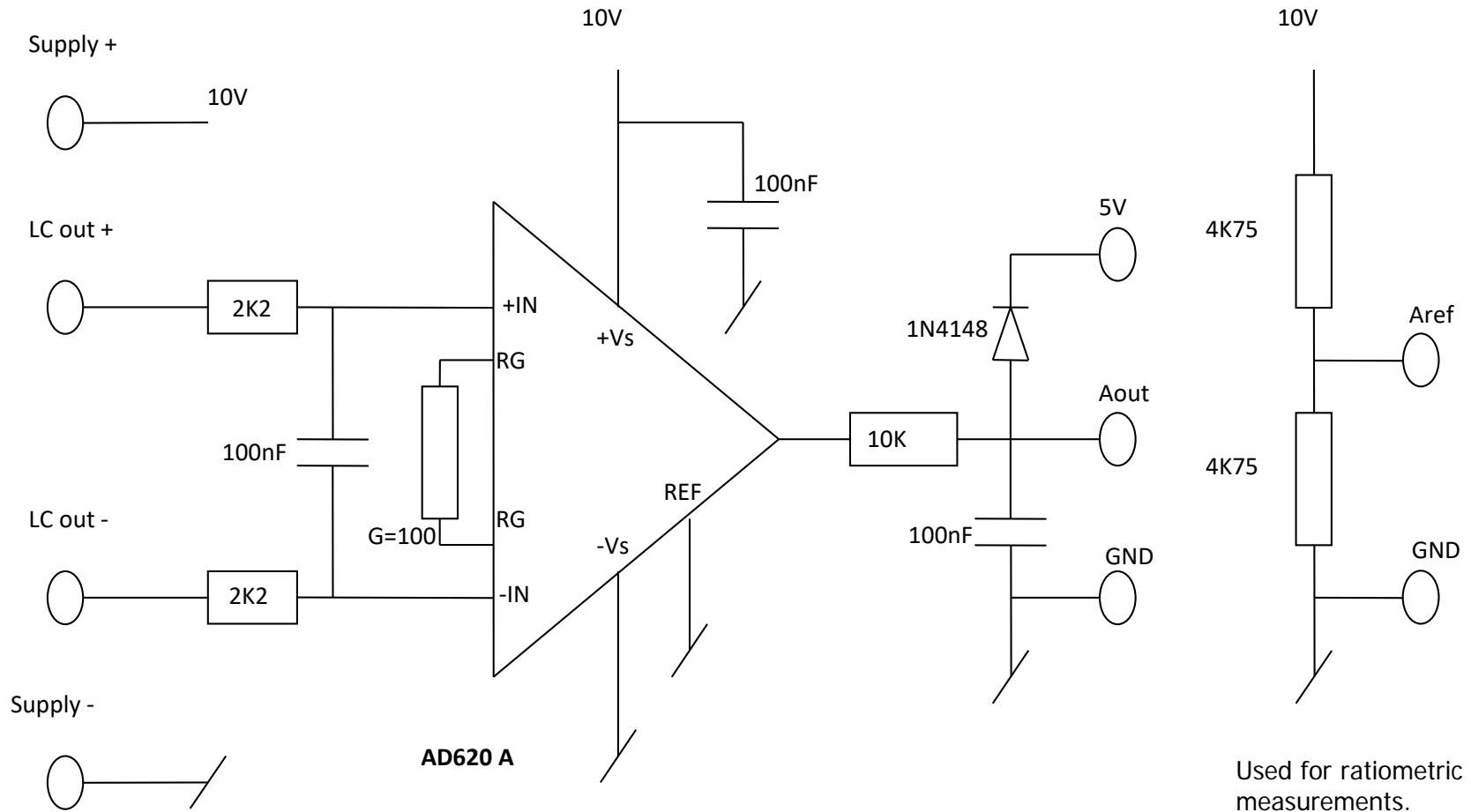

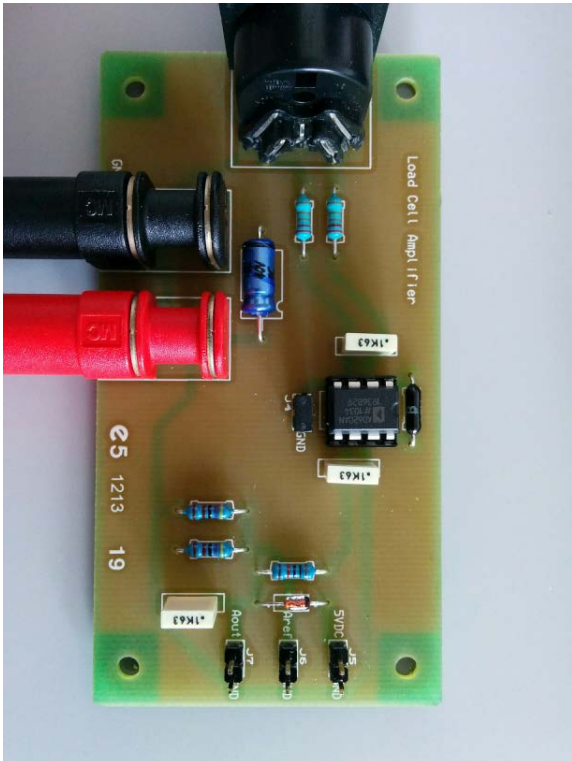- The load cell may need to be pre-loaded with a weight, to operate in its linear area.



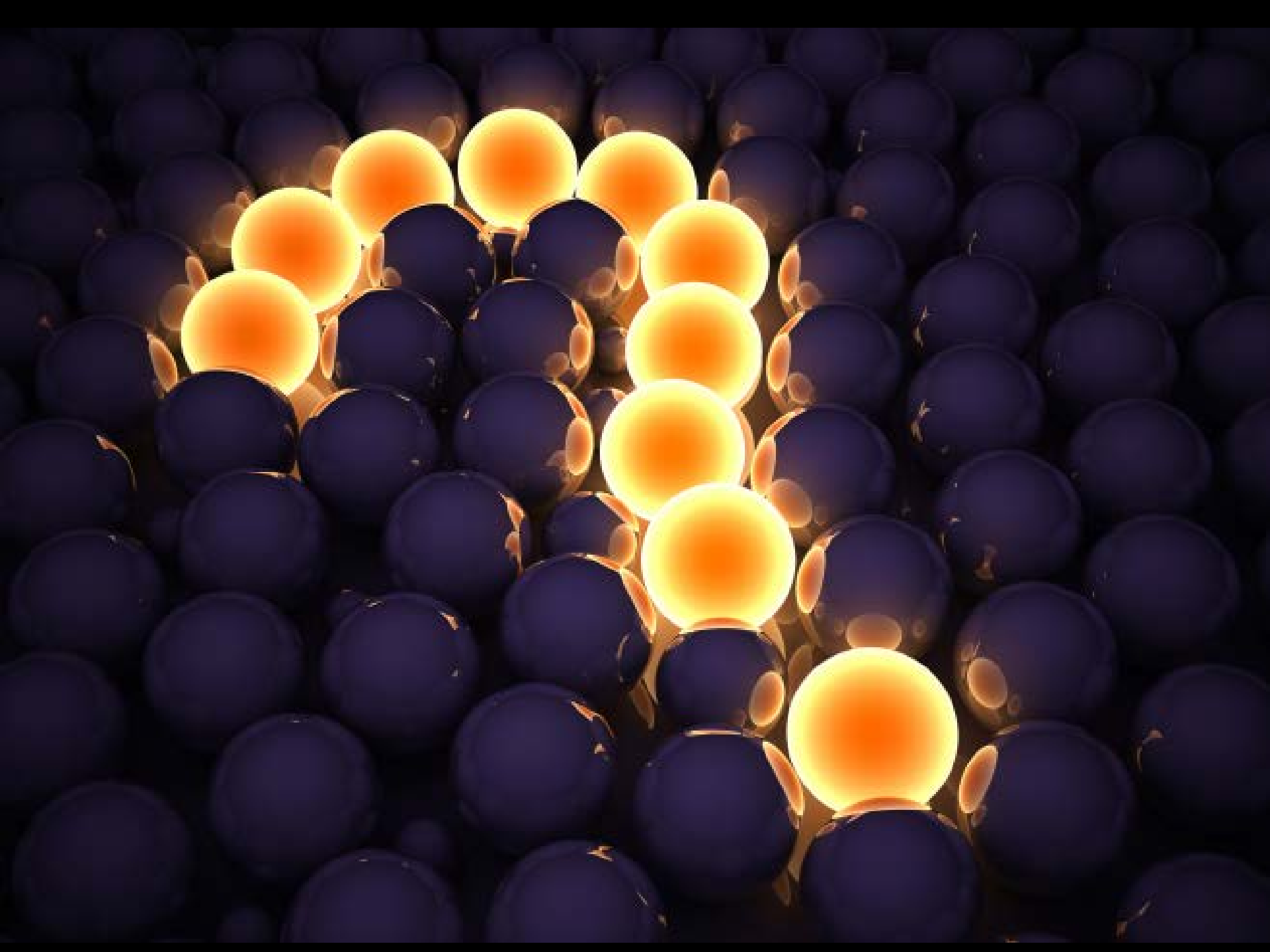- 
- You can use the provided PSoC project on Blackboard as a starting point.
  - It has a UART and a SAR ADC.



# Image resources

---

- Question mark: <https://wall.alphacoders.com/big.php?i=437563>