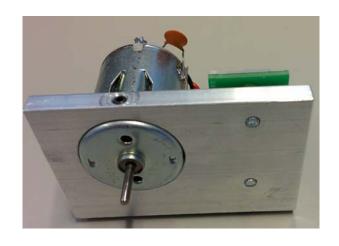


Motor control Lab experiment










3 experiments

- DC motor speed control with PWM.
- DC motor speed control with PWM and direction control with an H-Bridge.
- Stepper motor control.
- (+optional: Servo motor)




MOSFET PCB

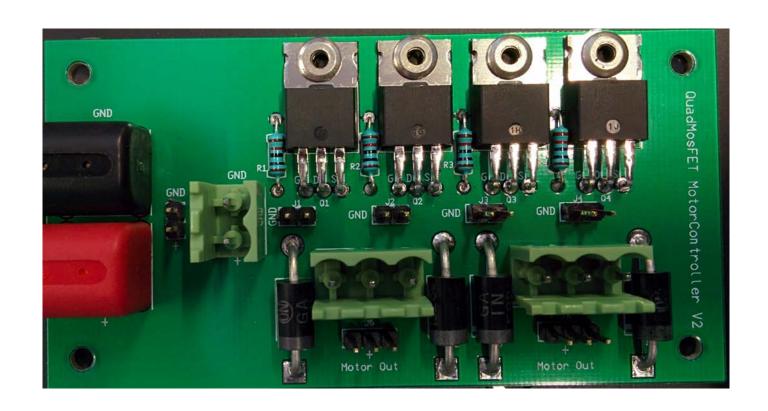



IRLZ24 N-channel MOSFET

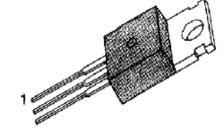


1. Gate 2. Drain 3. Source

Characteristic	Symbol	IRLZ24	IRLZ20	Unit
Drain-Source Voltage (1)	Voss	60	50	Vdc
Drain-Gate Voltage (Rgs=1MΩ)(1)	VDGR	60	50	Vdc
Gate-Source Voltage	Vgs	+	Adc	
Continuous Drain Current Tc=25 °C	lo	14.0		Adc
Continuous Drain Current Tc=100 °C	lo	9.8		Adc
Drain Current - Pulsed (3)	IDM	56		Adc
Total Power Dissipation @ Tc=25 °C	D-	5	Watts	
Derate Above 25 °C	PD	0.	w/°c	
Operating and Storage	T. T.	-55 to +175		• 0
Junction Temperature Range	Ту, Тятс			°C
Maximum Lead Temp. for Soldering	т.	300		
Purposes, 1/8" from case for 5 seconds	TL			°C



IRLZ24 N-channel MOSFET

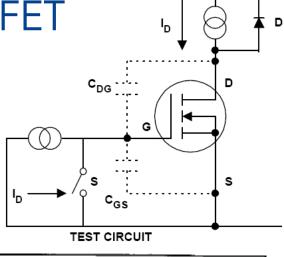

 V_{DD}


Symbol	Characteristic	Min	Тур	Max	Units	Test Conditions
BVoss	Drain-Source Breakdown Voltage					
	IRLZ24	60	-	-	v	Vgs=0V, lb=250µA
	IRLZ20	50	-	_	v	
VGS(th)	Gate Threshold Voltage	1.0	-	2.0	٧	VDS=VGS, ID=1mA
less	Gate-Source Leakage Forward	-	-	100	nΑ	Vgs=15V
lgss	Gate-Source Leakage Reverse	-	-	-100	nA	Vgs=-15V
loss Zer	Zero Gate Voltage Drain Current	-	-	250	μА	VDS=Max. Rating, VGS=0V
		-	-	1000	μΑ	Vos=0.8 Max. Rating, Vos=0V, Tc=125°C
RDS(on)	Static Drain-Source On-Resistance(2)	-	- (0.15	U	Vgs=5.0V, ID=7A
gfs	Forward Transconductance (2)	2.0	-	•	ซ	Vos≥15V, Io=7A



- There are two revisions of the MOSFET PCB. On the new revision of the PCB, the IRLZ24 is replaced by IRLZ44.
- For IRLZ44, the gate-threshold voltage can be up to 3V.
- So the PSoC shall use 5V logic, i.e. no modifications on the PSoC and set output to strong drive (the default).




MOS FET driver (LAB)

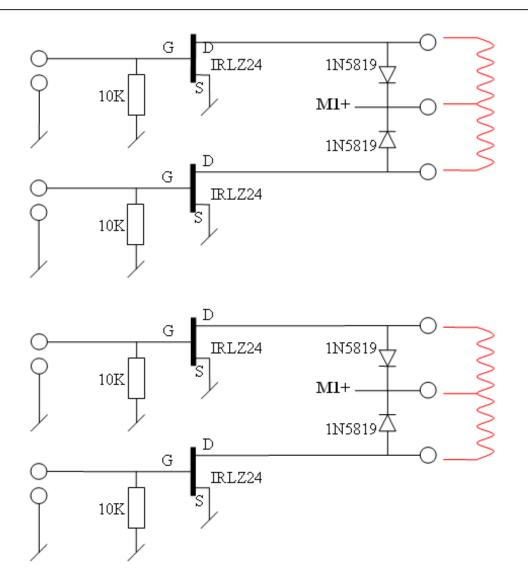




L298 PCB

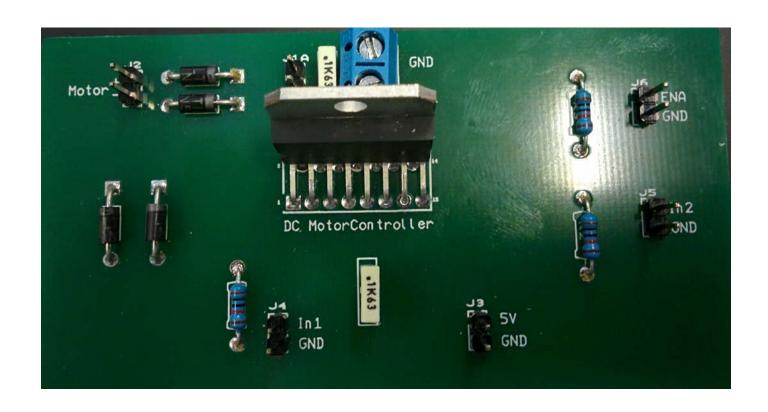




L298: Dual Full Bridae Driver

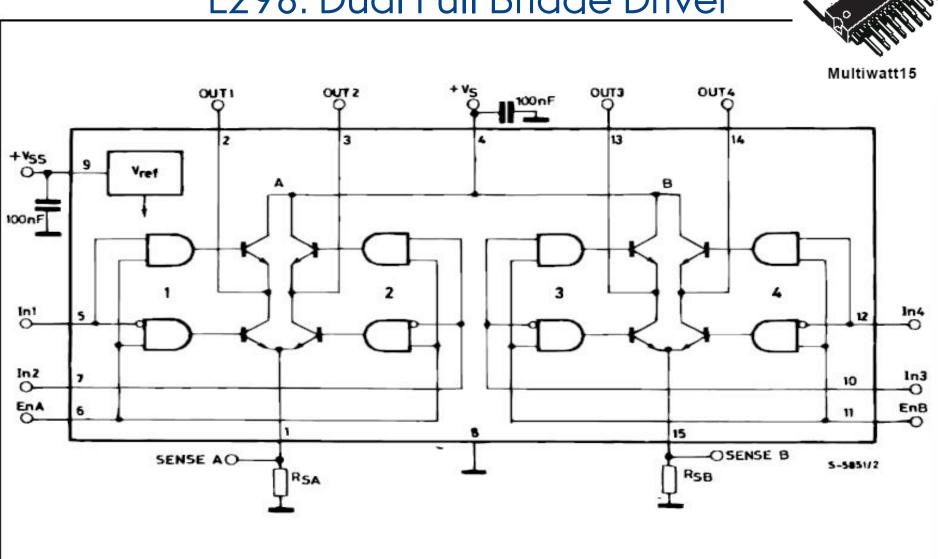





Lab H-Bridge

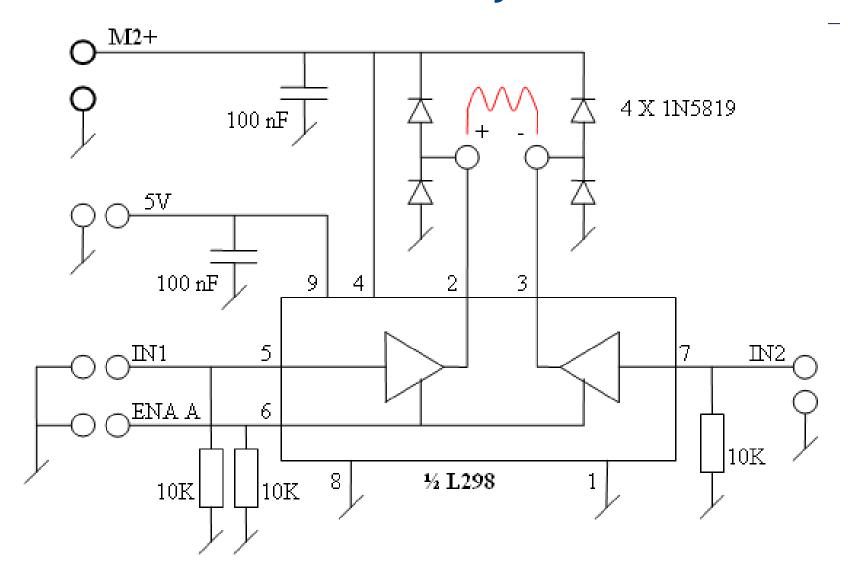




L298: Dual Full Bridge Driver

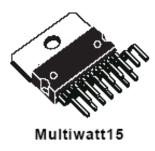

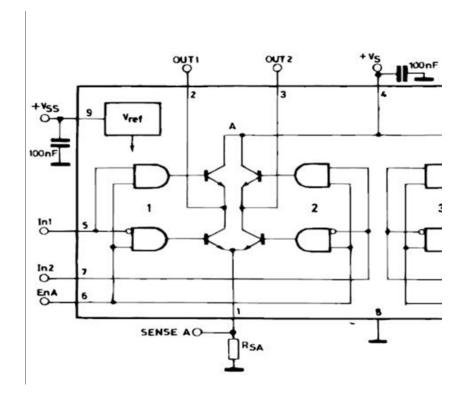

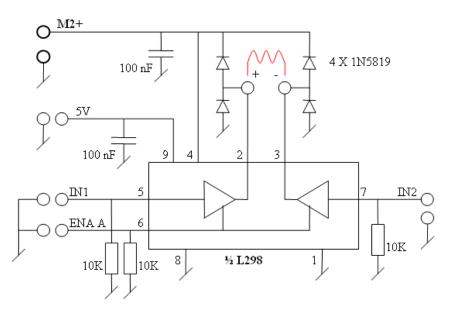



PSoC project on blackboard

- You can use the provided PSoC project on blackboard as a starting point.
- It has a UART and a PWM component.



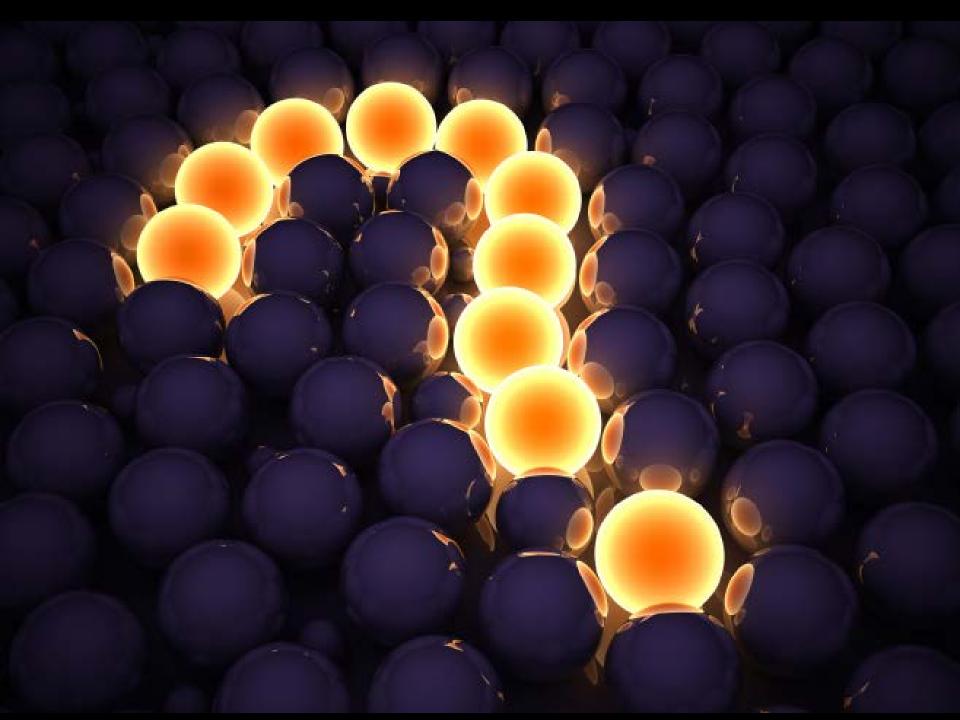


Image resources

Question mark: https://wall.alphacoders.com/big.php?i=437563

